

Construction of Electronic Systems

Exercise 8: USB DAQ project: SMPS design

By now you have made your initial component placement. Now you will design the *switched-mode power supply* (SMPS). First you will *analyze* the circuit and *identify the critical parts*. Then you will design the circuit on the PCB: you will make a *detailed component placement* and route the connections between the SMPS components, taking into account the *minimization of the electromagnetic interferences*.

Exercise tasks:

1. ***Before you start with the actual PCB design, make sure that you have the basic design rules properly set.*** Use the following settings:

- 1.1. board outline clearance: 0.5 mm

(Manufacturing → Board Outline Clearance → New rule)

- 1.2. minimal electrical clearance: 8 mil (Electrical → Clearance)

Option: use "Ignore Pad to Pad clearances within a footprint".

- 1.3. routing width: (Routing → Width)

1.3.1. minimal: 8 mil

1.3.2. preferred: 10 mil


1.3.3. maximal: 100 mil

- 1.4. via style: (Routing → Via Style)

	ring diameter [mm]	hole diameter [mm]
minimal	0.7	0.3
maximal	1.2	0.8
preferred	0.8	0.4

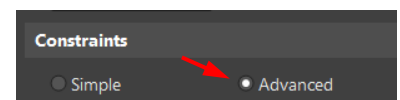
- 1.5 direct polygon connect to vias (Plane → Polygon Connect Style)

Hint: use the advanced configuration parameters.




2. ***Analyze the switched-mode power supply circuit and identify the critical circuit parts for both SEPIC and Ćuk power converters:***

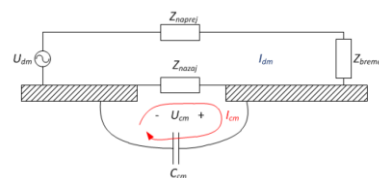- a) where do the *critical currents* flow, which are problematic because of their *high frequency spectrum*?
- b) The *area* of which *circuit loops* must be minimized in order to minimize the *differential mode interferences*?
- c) Where can the *currents* generate the *common mode interferences*? What can be done to minimize these interferences?



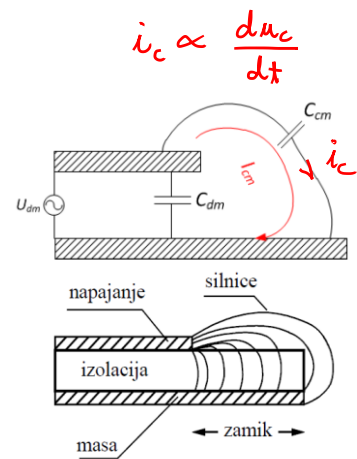- d) In which circuit nodes do the *critical voltages* appear which are problematic because of their *high frequency spectrum*?
- e) Where can the *voltages* generate the *common mode* interferences? What can be done to minimize these interferences?



Advice: use the power converter *simulations* (links above) and the IC application note (see attachments eFE folder).

3. Design the switched-mode power supply, taking into account the identified critical circuit parts.

Use the knowledge and understanding of the circuit critical parts to produce a good power supply design. Start with a *detailed SMPS component placement*, trying to *minimize the critical circuit loops*. Also, try to place the components in such a way that the *critical ground return path impedance* is minimized.

Tip: place the critical components first and then proceed to the less critical.

Tip: First, make the component placement and only then start connecting the components.

Explanation of the exercise

Before you start with the *more detailed design of the individual circuit parts*, you should define the most fundamental design rules that dictate how the components can be *placed* (e.g. required edge clearance) and how can they be *connected* (e.g. track width limitations).

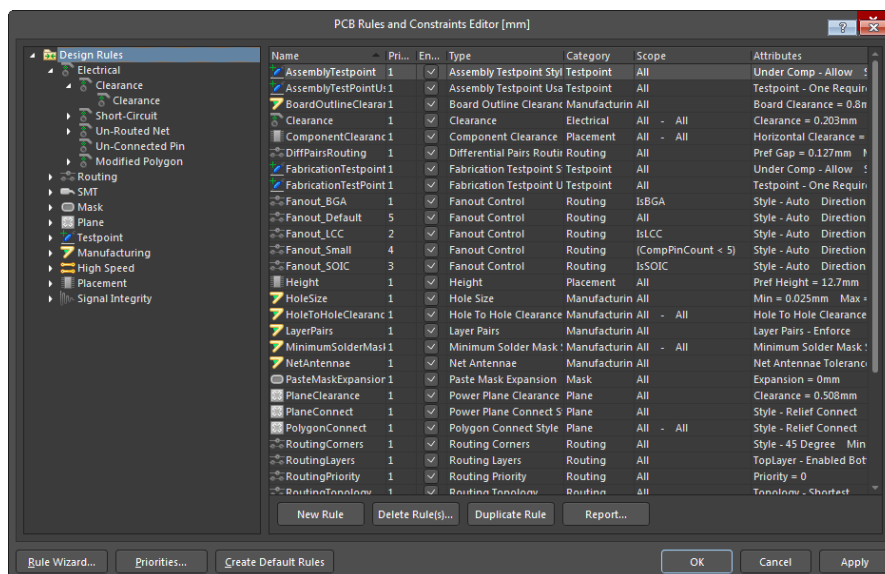


Figure 1 - setting the basic design rules before you start with a more detailed PCB design. The number of the available design rules can be a bit terrifying.

After you have made the initial component placement and prepared the basic design rules, you can start with the *detailed design of the individual electrical circuit parts*. In our case, you will start with the switched-mode power supply part. In order to make a good SMPS design, you need *to understand the way this circuit works, so that the critical parts will be easier to identify and taken care for*.

SMPS for split Analog Power Supply (APS)

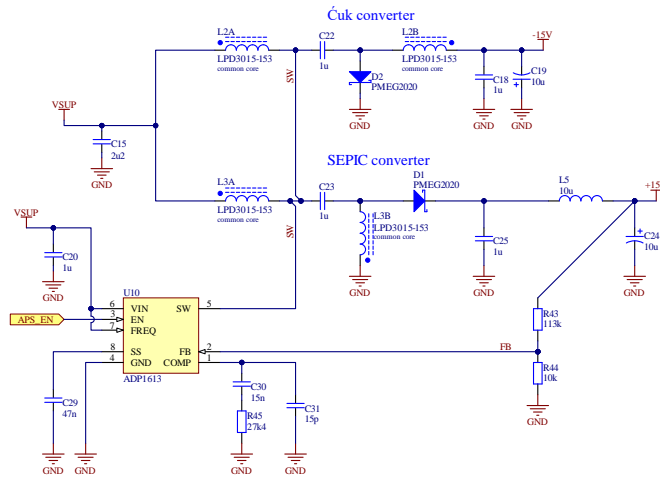


Figure 2 – you will design the switched-mode power supply for the analog circuitry

Preparation for the lab exercise

You will finally start designing the PCB so it makes sense to familiarize yourself with the [useful functions and shortcuts in PCB](#).